

# IT FUNDAMENTALS

## Week 2 – Digital Circuits

---

### Assignment 2.1: Parking lot

Er zijn **3** parkeerplaatsen.

Als **alle 3 bezet zijn**, moet het bord **FULL** laten zien.

#### a) What logic gate(s) do you need to make this circuit?

Hiervoor heb je een **AND-gate** nodig.

#### Uitleg:

Alleen als **parking lot 1**, **parking lot 2** én **parking lot 3** bezet zijn (allemaal 1), mag de uitkomst **FULL = 1** zijn.

#### b) Truth table

Parking lot 1	Parking lot 2	Parking lot 3	Result (FULL)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Alleen wanneer **alle drie** de parkeerplaatsen bezet zijn, is de parkeerplaats **vol**.

## Assignment 2.2: Android phone or iPhone?

Een werknemer kan **maar één telefoon** kiezen:

- Android **of**
  - iPhone
- Niet allebei tegelijk.

### a) What logic gate do you need to make this circuit?

Hiervoor gebruik je een **XOR-gate**.

#### Uitleg:

Een XOR-gate geeft alleen een **1** als **exact één** invoer 1 is.

### b) Truth table

Android phone	iPhon e	Result (phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Als beide 1 zijn, is de uitkomst 0, omdat je **niet beide telefoons tegelijk** mag hebben.

## Assignment 2.3: Four NAND gates

Een NAND-gate is het tegenovergestelde van een AND-gate.

### Truth table

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

## Simplification of the chip design

Een circuit dat bestaat uit **meerdere NAND-gates** kan vaak worden vereenvoudigd tot:

- een **AND-gate**
- een **OR-gate**
- of een **NOT-gate**


Dit is mogelijk omdat **NAND-gates universeel zijn**:

je kunt **alle andere logic gates** bouwen met alleen NAND-gates.

## Assignment 2.4: Becoming familiar with Logisim Evolution

Screenshot of the design with your name and student number in it:


**Nabil Elbaze 572191**

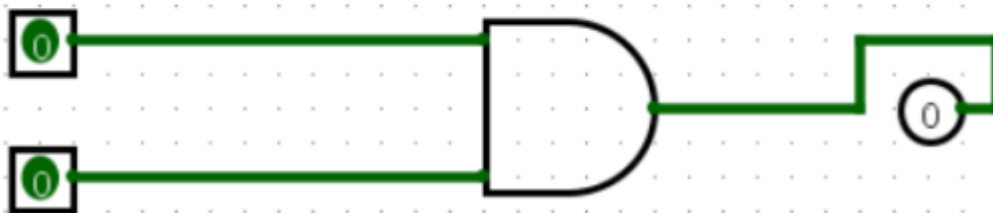

## Assignment 2.5: Create an SR Latch in Logisim

Screenshot of the design with your name and student number in it:


**Nabil Elbaze 572191**

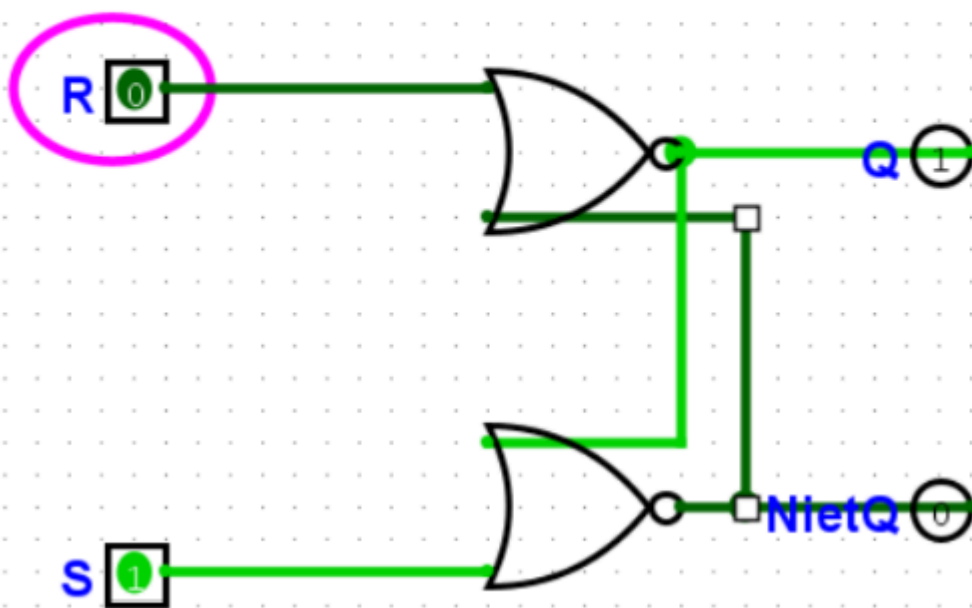

## Assignment 2.6: Create a Vending Machine

Screenshot of the design with your name and student number in it:

**Nabil Elbaze 572191**

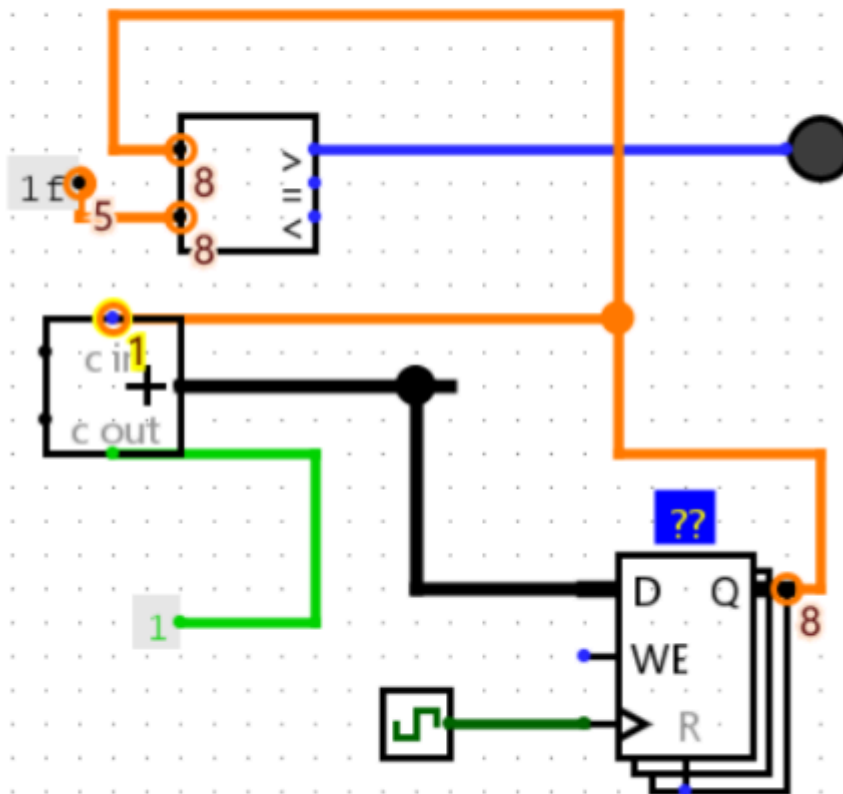

## Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
public class BitwiseAssignment {

    public static void main(String[] args) {

        int studentNumber = 572191;

        int example = 0b1111; // as a example

        // Bitwise AND

        int andResult = studentNumber & example;

        // Bitwise OR

        int orResult = studentNumber | mask;

        // Bitwise XOR

        int xorResult = studentNumber ^ mask;

        System.out.println("AND result: " + andResult);

        System.out.println("OR result: " + orResult);

        System.out.println("XOR result: " + xorResult); } }
```

## Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Paste source code here, with a screenshot of a working application.

```
import java.util.Scanner;
```

```
public class Main {  
  
    public static void main(String[] args) {  
  
        Scanner scanner = new Scanner(System.in);  
  
        System.out.println("\nMenu:");  
  
        System.out.println("1. Is number odd?");  
  
        System.out.println("2. Is number a power of 2?");  
  
        System.out.println("3. Two's complement of number");  
  
        System.out.println("4. Exit");  
  
        System.out.print("Enter your choice: ");  
  
        int choice = scanner.nextInt();  
  
        if (choice == 4) {  
  
            System.out.println("Exiting the program. Goodbye!");  
  
            return;  
  
        }  
  
        System.out.print("Enter a number: ");  
  
        int number = scanner.nextInt();  
  
        if (choice == 1) {  
  
            boolean isOdd = (number & 1) == 1;  
  
            System.out.println("The number " + number + (isOdd ? " is odd." : " is even."));  
  
        } else if (choice == 2) {  
  
            boolean isPowerOfTwo = number > 0 && (number & (number - 1)) == 0;  
  
            System.out.println("The number " + number + (isPowerOfTwo ? " is a power of 2." : " is not a  
power of 2."));  
  
        } else if (choice == 3) {  
  
            int twosComplement = ~number + 1;  
  
            System.out.println("The two's complement of " + number + " is: " + twosComplement);  
  
        }  
  
    }  
}
```

```

} else {

System.out.println("Invalid choice. Please try again.");

}

scanner.close();

}

}

```

Screenshot optie 1:

The screenshot shows an IDE with a Java file named `Main.java`. The code implements a menu-driven program with the following logic:

- Menu:**
  - 1. Is number odd?
  - 2. Is number a power of 2?
  - 3. Two's complement of number
  - 4. Exit
- Execution Flow:**
  - The user enters `1` as a choice.
  - The program prompts: `Enter a number: 5`.
  - The user enters `5`.
  - The program outputs: `The number 5 is even.`
  - The process finishes with exit code 0.

The Java code in `Main.java` is as follows:

```

public class Main {
    public static void main(String[] args) {
        Scanner scanner = new Scanner(System.in);

        System.out.println("Menu:");
        System.out.println("1. Is number odd?");
        System.out.println("2. Is number a power of 2?");
        System.out.println("3. Two's complement of number");
        System.out.println("4. Exit");
        System.out.print("Enter your choice: ");

        int choice = scanner.nextInt();

        if (choice == 4) {
            System.out.println("Exiting the program. Goodbye!");
            return;
        }


        System.out.print("Enter a number: ");
        int number = scanner.nextInt();

        if (choice == 1) {
            boolean isOdd = (number & 1) == 1;
            System.out.println("The number " + number + " is odd." + (isOdd ? " : " : " is even."));
        } else if (choice == 2) {
            boolean isPowerOfTwo = number > 0 && (number & (number - 1)) == 0;
            System.out.println("The number " + number + " is a power of 2." + (isPowerOfTwo ? " : " : " is not a power of 2."));
        } else if (choice == 3) {
            int twoComplement = ~number + 1;
            System.out.println("The two's complement of " + number + " is: " + twoComplement);
        }
    }
}

```



screenshot 2:

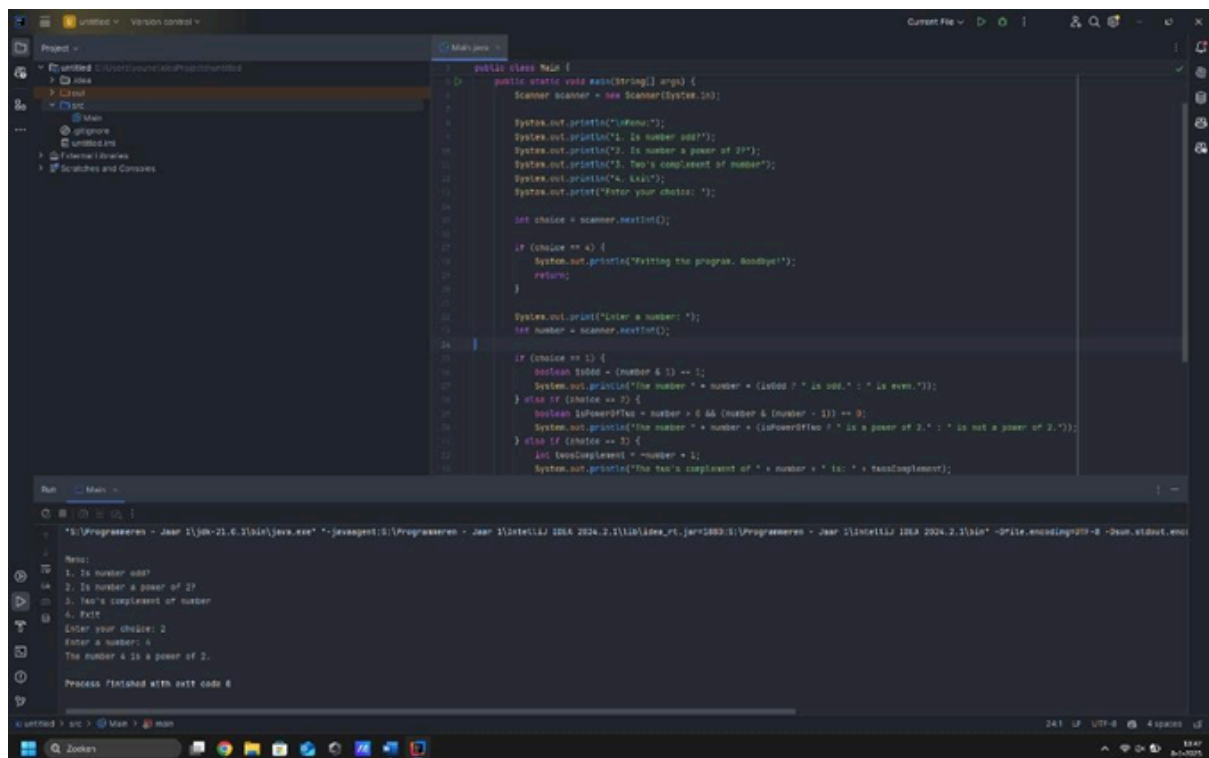


```
public class Main {  
    public static void main(String[] args) {  
        Scanner scanner = new Scanner(System.in);  
  
        System.out.println("Welcome");  
        System.out.println("1. Is number odd?");  
        System.out.println("2. Is number a power of 2?");  
        System.out.println("3. Two's complement of number");  
        System.out.println("4. Exit");  
        System.out.print("Enter your choice: ");  
  
        int choice = scanner.nextInt();  
  
        if (choice == 4) {  
            System.out.println("Exiting the program. Goodbye!");  
            return;  
        }  
  
        System.out.print("Enter a number: ");  
        int number = scanner.nextInt();  
  
        if (choice == 1) {  
            boolean isOdd = (number & 1) == 1;  
            System.out.println("The number " + number + (isOdd ? " is odd." : " is even."));  
        } else if (choice == 2) {  
            boolean isPowerOfTwo = number > 0 && (number & (number - 1)) == 0;  
            System.out.println("The number " + number + (isPowerOfTwo ? " is a power of 2." : " is not a power of 2."));  
        } else if (choice == 3) {  
            int twoComplement = ~number + 1;  
            System.out.println("The two's complement of " + number + " is: " + twoComplement);  
        }  
    }  
}
```

Run - Main -

1. Is number odd?  
2. Is number a power of 2?  
3. Two's complement of number  
4. Exit  
Enter your choice: 2  
Enter a number: 4  
The number 4 is a power of 2.  
Process finished with exit code 0

screenshot 3:

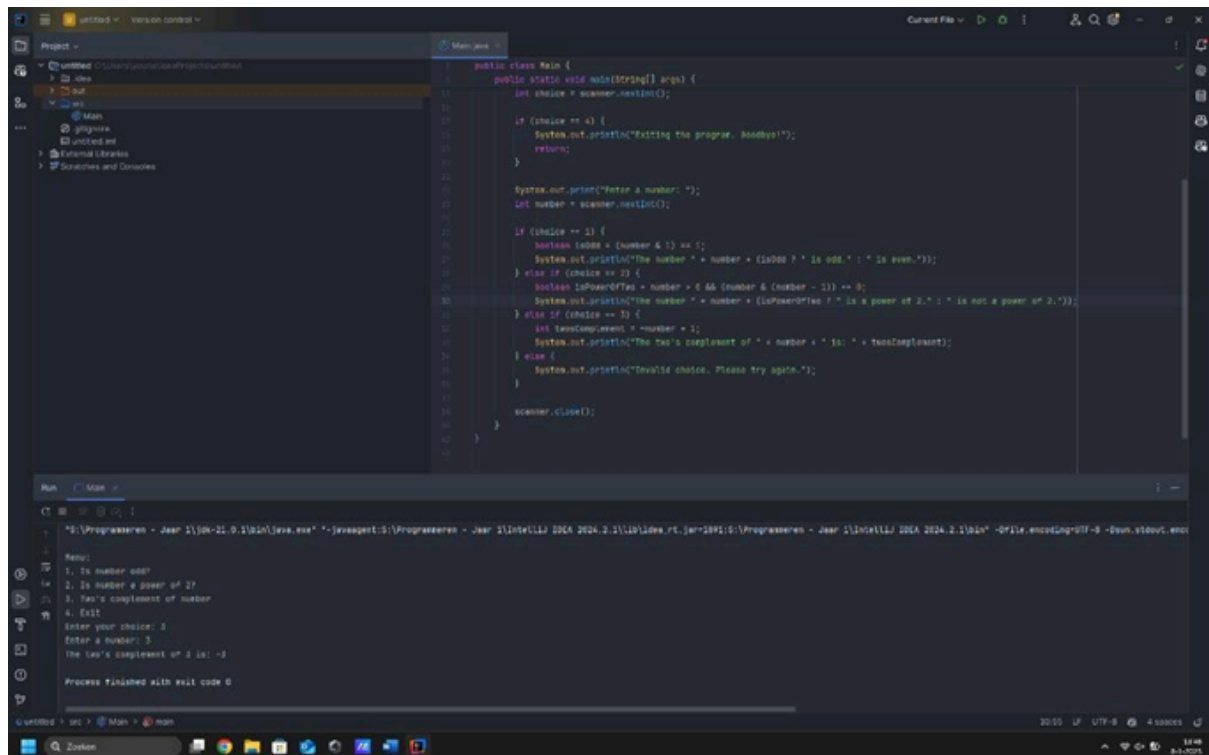

```
public class Main {  
    public static void main(String[] args) {  
        int choice = scanner.nextInt();  
  
        if (choice == 4) {  
            System.out.println("Exiting the program. Goodbye!");  
            return;  
        }  
  
        System.out.print("Enter a number: ");  
        int number = scanner.nextInt();  
  
        if (choice == 1) {  
            boolean isOdd = (number & 1) == 1;  
            System.out.println("The number " + number + (isOdd ? " is odd." : " is even."));  
        } else if (choice == 2) {  
            boolean isPowerOfTwo = number > 0 && (number & (number - 1)) == 0;  
            System.out.println("The number " + number + (isPowerOfTwo ? " is a power of 2." : " is not a power of 2."));  
        } else if (choice == 3) {  
            int twoComplement = ~number + 1;  
            System.out.println("The two's complement of " + number + " is: " + twoComplement);  
        } else {  
            System.out.println("Invalid choice. Please try again.");  
        }  
  
        scanner.close();  
    }  
}
```

Run - Main -

1. Is number odd?  
2. Is number a power of 2?  
3. Two's complement of number  
4. Exit  
Enter your choice: 3  
Enter a number: 3  
The two's complement of 3 is: -4  
Process finished with exit code 0